

Analogue Electronics

Xiping Hu

<https://hxp.plus/>

Contents

1	Basics of Circuits	5
1.1	The direction of current and voltage	5
1.2	How to determine whether a component is consuming or providing energy	5
1.3	Electronic Components	5
1.3.1	Resistors	5
1.3.2	Power Sources	5
1.4	Kirchhoff's Laws	6
1.4.1	Kirchhoff's Current Law	6
1.4.2	Kirchhoff's Voltage Law	6
2	Operational Amplifier	7
2.1	Operational Amplifier	7
2.2	Ideal Operational Amplifier	7
2.3	Closed-looped Amplifier	8
2.3.1	Non-inverting Operational Amplifier	8
2.3.2	Inverting Operational Amplifier	9
2.4	Applications of operational amplifiers	9
2.4.1	Subtraction Circuit	9
2.4.2	Sum Circuit	10
2.4.3	Integrating Circuit	11
2.4.4	Differential Circuit	12
3	Diodes	13
3.1	Semiconductors	13
3.1.1	Intrinsic Semiconductor	13
3.1.2	Extrinsic Semiconductor	13
3.2	P-N Junction and Diode	13
3.2.1	Breakdown of P-N Junction	14
3.3	Diode modeling	14
3.3.1	Mathematically idealized diode	14
3.3.2	Ideal diode in series with voltage source	15
3.3.3	Diode with voltage source and current-limiting resistor	15
3.3.4	Diode in Small Signal Circuits	16
3.4	Applications of Diodes	16
3.4.1	Rectifier Circuit	16
3.4.2	Limiting Circuit	17
3.4.3	Switching Circuit	17
3.5	Diodes for Special Usage	17
3.5.1	Zener diode	17
3.5.2	Photodiode	17
3.5.3	Light-emitting diode	17
3.5.4	Schottky diode	18
4	MOSFET and Amplifying Circuit	19

4.1	Classification of MOSFET	19
4.1.1	N-type Enhancement-mode MOSFET	19
4.1.2	N-type Depletion-mode MOSFET	20
4.1.3	P-type MOSFET	21
4.2	Static Working Point	22
4.3	Early Effect	22
4.4	Three types of Amplifier Circuit	23
4.4.1	Common Source Amplifier Circuit	23
4.4.2	Common Drain Amplifier Circuit	24
4.4.3	Common Gate Amplifier Circuit	25
5	Bipolar Junction Transistor	27
5.1	Control Principle	27
5.2	Three Types of Amplifier Circuit	27
5.3	Static Working Point	28
5.4	Model of Small Signal	28
5.5	Compound Transistor	29

Chapter 1

Basics of Circuits

1.1 The direction of current and voltage

In complex problems, we can not always know the direction of currents or voltage. The usual solution is to assume a direction, and use it to solve problems. If the solution of current or voltage, is positive, then the position is just what we assumed, and vice versa.

1.2 How to determine whether a component is consuming or providing energy

For resistors, resistors are always consuming energy.

For power sources, if the direction of current is from the positive electrode to the negative electrode, then the power source is consuming energy, and vice versa.

1.3 Eletronic Components

1.3.1 Resistors

$$U = -IR$$

1.3.2 Power Sources

(Controlled) Voltage Source

$$P = UI$$

The resistance of an ideal voltage source is : 0

Note that an ideal voltage source must not be short-circuited.

(Controlled) Current Source

The current through a current source is only decided by the source itself.

The resistance of an ideal current source is : ∞

Note that an ideal current source must not be open-circuited.

1.4 Kirchhoff's Laws

- branch
- node
- loop
- mesh

1.4.1 Kirchhoff's Current Law

For each node in the circuit, as the node can not accumulate charges, the sum of current is zero.

$$\sum I = 0$$

1.4.2 Kirchhoff's Voltage Law

For each loop in circuit, the sum of the voltage in of all branches is zero.

$$\sum U = 0$$

Chapter 2

Operational Amplifier

2.1 Operational Amplifier


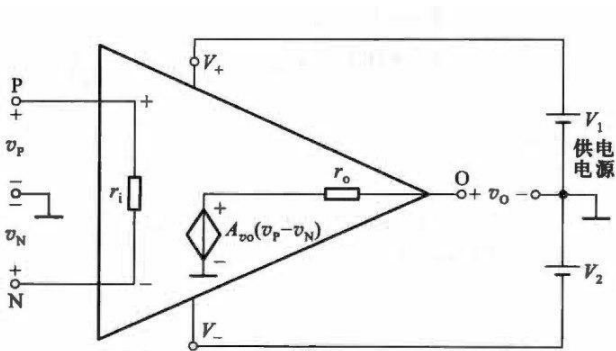


图 2.1.3 运算放大器的电路简化模型

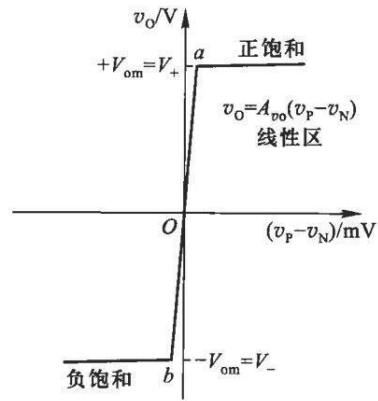(a) the model of an operational amplifier



(b) How the output voltage varies

Figure 2.1

We define r_i as the input impedance, r_o as the output impedance. v_p as the non-inverting input, v_n the inverting input.

Usually, we have $v_p \approx v_n$, $r_i \approx \infty$, $r_o \approx 0$.

Note that the output voltage of a operational amplifier has limits, called **Bandwidth**. When the input voltage exceeds the limits, it outputs the maximum or minimum value.

2.2 Ideal Operational Amplifier

For ideal operational amplifier:

- $v_p = v_n$, $i_i = 0$, $r_i = \infty$
- $r_o = 0$, $v_o = A_{vo}(v_p - v_n)$
- $bandwidth = \infty$

Here is a model which shows all the feature of an ideal operational comparator:

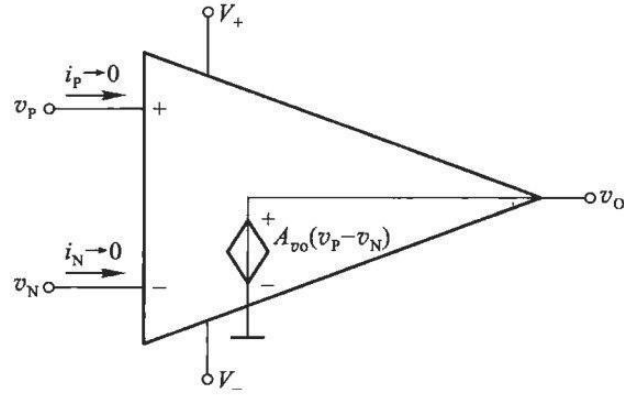


Figure 2.2: An ideal operational amplifier

2.3 Closed-loop Amplifier

Usually operational amplifiers are used with vegetative feedback to ensure its stability. We apply a portion of output voltage to input, reducing the gain of a circuit.

2.3.1 Non-inverting Operational Amplifier

If we connect the inverting input, to the ground, and use the non-inverting input, we get an non-inverting operational amplifier.

The gain of the amplifier is:

$$A_{vo} = \frac{R_2 + R_1}{R_1}$$

The picture below is a non-inverting amplifier.

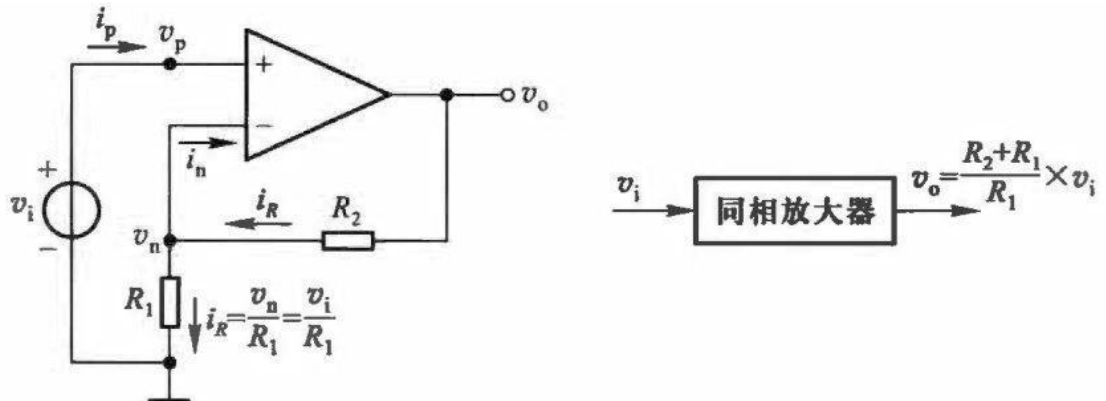


Figure 2.3: An non-inverting amplifier

$$\begin{cases} i_R = \frac{v_o - v_n}{R_2} = \frac{v_n}{R_1} \\ v_n = v_p = v_i \end{cases}$$

$$\frac{v_o - v_n}{R_2} = \frac{v_i}{R_1}$$

$$A_v = \frac{v_o}{v_i} = \frac{R_1 + R_2}{R_1}$$

Note that when $R_2 \ll R_1$, $A_{vo} = 1$, $v_i = v_o$.

2.3.2 Inverting Operational Amplifier

If we connect the non-inverting input, to the ground, and use the inverting input, we get an inverting operational amplifier.

The gain of this type of amplifier is:

$$A_{vo} = -\frac{R_2}{R_1}$$

The picture below shows as inverting operational amplifier:

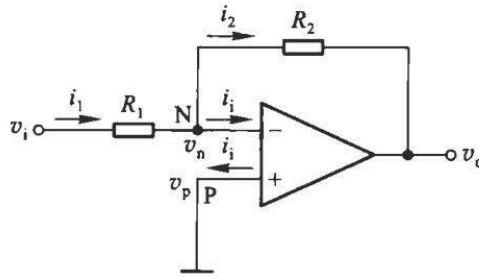


Figure 2.4: An inverting amplifier

$$\begin{cases} \frac{v_o - v_n}{R_2} = \frac{v_n - v_i}{R_1} \\ v_n = v_p = 0 \end{cases}$$

$$\frac{v_o}{R_2} = \frac{-v_i}{R_1}$$

$$A_v = \frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

2.4 Applications of operational amplifiers

2.4.1 Subtraction Circuit

An subtraction circuit can calculate the difference of inverting input and non-inverting input.

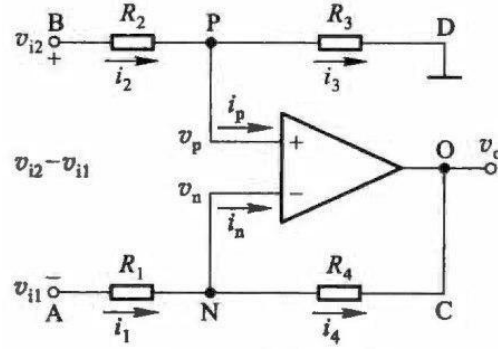


Figure 2.5: A subtraction circuit

$$\begin{cases} \frac{v_{i2} - v_p}{R_2} = \frac{v_p}{R_3} \\ \frac{v_{i1} - v_n}{R_1} = \frac{v_n - v_o}{R_4} \end{cases}$$

$$\begin{cases} R_3(v_{i2} - v_p) = R_2 v_p & \Rightarrow v_p = \frac{R_3}{R_2 + R_3} v_{i2} \\ R_4(v_{i1} - v_n) = R_1(v_n - v_o) & \Rightarrow v_n = \frac{R_4 v_{i1} + R_1 v_o}{R_4 + R_1} \end{cases}$$

$$\frac{R_3}{R_2 + R_3} v_{i2} = \frac{R_4 v_{i1} + R_1 v_o}{R_4 + R_1}$$

$$\frac{R_3(R_4 + R_1)}{R_2 + R_3} v_{i2} = R_4 v_{i1} + R_1 v_o$$

\Rightarrow

$$v_o = \frac{\frac{R_4}{R_1} + 1}{\frac{R_2}{R_3} + 1} v_{i2} - \frac{R_4}{R_1} v_{i1} = \left(1 + \frac{R_4}{R_1}\right) \frac{\frac{R_3}{R_2}}{1 + \frac{R_3}{R_2}} v_{i2} - \frac{R_4}{R_1} v_{i1}$$

If $R_4/R_1 = R_3/R_2 = r$, then

$$v_o = (1 + r) \frac{r}{1 + r} v_{i2} - r v_{i1} = r(v_{i2} - v_{i1})$$

$$A_v = r = \frac{R_4}{R_1} = \frac{R_3}{R_2}$$

2.4.2 Sum Circuit

An sum circuit adds the inverting input and the non-inverting input.

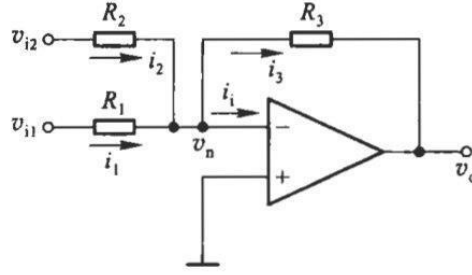


Figure 2.6: Sum Circuit

Similarly, we have

$$\begin{cases} \frac{v_{i1} - v_n}{R_1} + \frac{v_{i2} - v_n}{R_2} = \frac{v_n - v_o}{R_3} \\ v_n = v_p = 0 \end{cases}$$

\Rightarrow

$$\frac{v_{i1}}{R_1} + \frac{v_{i2}}{R_2} = \frac{-v_o}{R_3}$$

$$v_o = -\left(\frac{R_3}{R_1}v_{i1} + \frac{R_3}{R_2}v_{i2}\right)$$

When we set

$$R_1 = R_2 = R_3$$

We have

$$v_o = -(v_{i1} + v_{i2})$$

2.4.3 Integrating Circuit

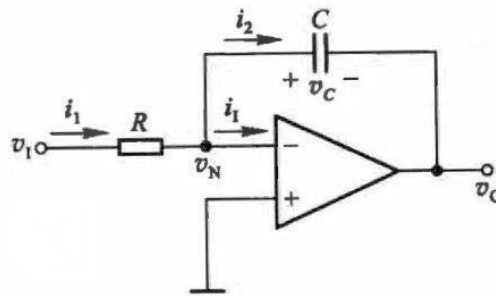


Figure 2.7: integrating circuit

$$C = \frac{Q}{U} \Rightarrow U = \frac{Q}{C} = \frac{1}{C} \int I dt = \frac{1}{C} \int \frac{v_i}{R} dt = \frac{1}{RC} \int v_i dt$$

$$0 - v_o = U$$

\Rightarrow

$$v_o = -\frac{1}{RC} \int v_i dt$$

We define

$$\tau = RC$$

Then

$$-v_o = \frac{1}{\tau} \int v_i dt$$

2.4.4 Differential Circuit

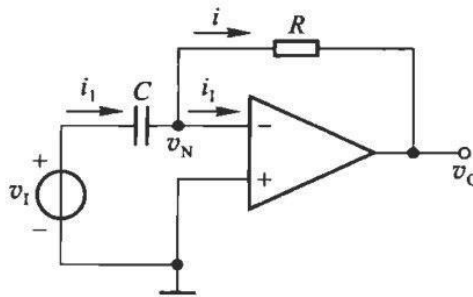


Figure 2.8: differential circuit

$$\begin{cases} i_i = \frac{dQ}{dt} = C \frac{dv_i}{dt} \\ i = \frac{v_o}{R} \\ i_i = i \end{cases}$$

\Rightarrow

$$-v_o = RC \frac{dv_i}{dt} = \tau \frac{dv_i}{dt}$$

Chapter 3

Diodes

3.1 Semiconductors

3.1.1 Intrinsic Semiconductor

An intrinsic semiconductor, also called as undoped semiconductor, is a pure semiconductor without and significant dopant species present. Two factors are responsible to the current pass through it:

- Excited electrons
- Holes

However, we seldom use intrinsic semiconductors.

3.1.2 Extrinsic Semiconductor

An extrinsic semiconductor is a semiconductor that has been doped, which has more features and provides more charge carriers.

P-type semiconductor

P-type semiconductors are created by doping some electron acceptor elements during manufacture. It has more holes, holes are major carriers of the current.

N-type semiconductor

N-type semiconductors are created by doping some electron donor elements during manufacture. It has more electrons, electrons are major carriers of the current.

3.2 P-N Junction and Diode

When we combine the 2 types of extrinsic semiconductor together, we found some interesting features. As p-type semiconductors use holes to transmit currents, n-type semiconductors use electrons to transmit currents, and, to make life easier, we take holes as positive charges. When the two types of semiconductors are put together, at the contact surface, diffusion phenomenon occur.

Some holes traveled into the n-type semiconductor, some electrons traveled into the p-type semiconductor. And after that, an inner electric field formed, which hinders the p-n junction from carrying currents.

To ease the effect above, we need to add some positive voltage at p-type semiconductor, and also add some negative voltage at n-type semiconductor. And if we add negative voltage at n-type semiconductor, positive voltage at p-type semiconductor, the effect will be intensified.

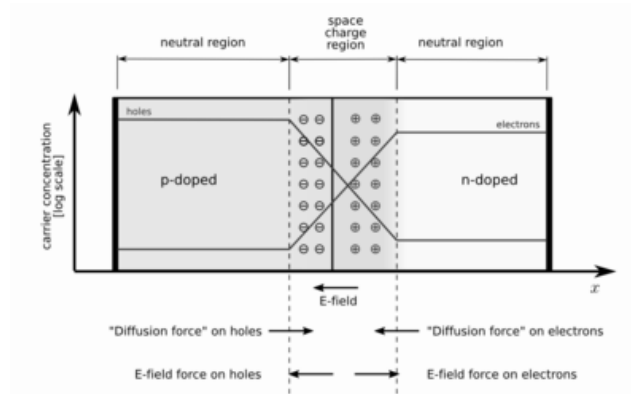


Figure 3.1: PN Junction at equilibrium state

In conclusion, if we add forward voltage (from p to n), the diode acts as a short circuit. If we add reversed voltage, the diode acts like an open circuit. And if the reversed voltage is big enough, it will cause the diode broken-through, and the current flow through it will increase tremendously.

3.2.1 Breakdown of P-N Junction

There are two types of breakdown

- electricity breakdown, which is invertible
- heat breakdown, which cause permanent damage

3.3 Diode modeling

3.3.1 Mathematically idealized diode

Firstly, consider a mathematically idealized diode. In such an ideal diode, if the diode is reverse biased, the current flowing through it is zero. This ideal diode starts conducting at 0 V and for any positive voltage an infinite current flows and the diode acts like a short circuit. The I-V characteristics of an ideal diode are shown below:


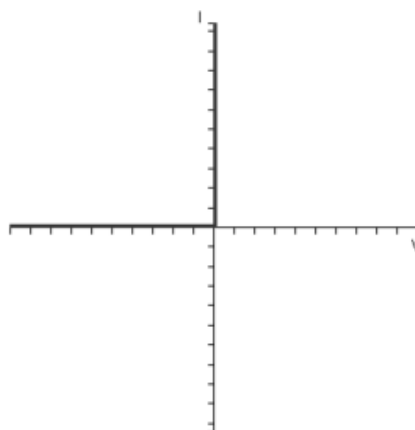


Figure 3.2: I-V characteristic of an ideal diode.

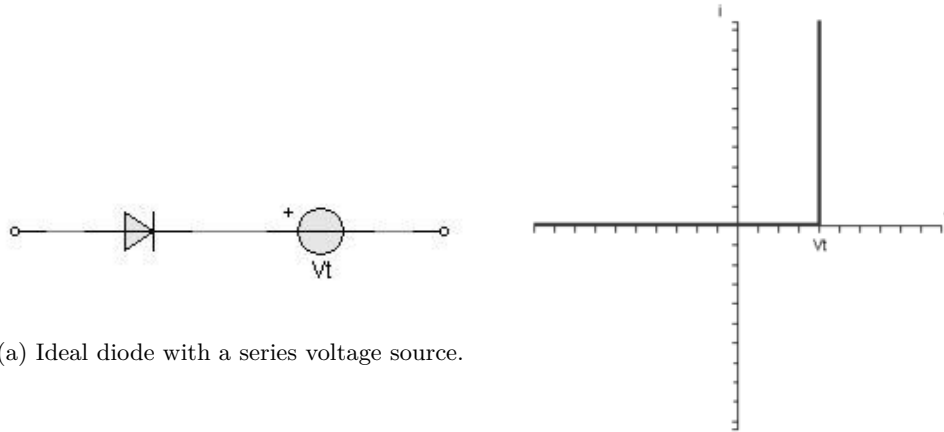3.3.2 Ideal diode in series with voltage source

Now consider the case when we add a voltage source in series with the diode in the form shown below:

When forward biased, the ideal diode is simply a short circuit and when reverse biased, an open circuit.




(a) Ideal diode with a series voltage source.

(b) I-V characteristic of an ideal diode with a series voltage source.

Figure 3.3: Ideal diode in series with voltage source

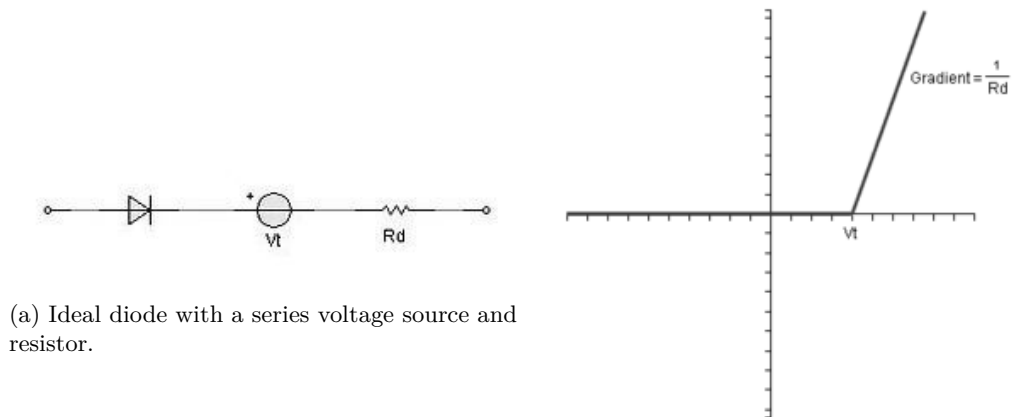3.3.3 Diode with voltage source and current-limiting resistor

The last thing needed is a resistor to limit the current, as shown below:



(a) Ideal diode with a series voltage source and resistor.

(b) I-V characteristic of an ideal diode with a series voltage source and resistor.

Figure 3.4: Diode with voltage source and current-limiting resistor

The real diode now can be replaced with the combined ideal diode, voltage source and resistor and the circuit then is modelled using just linear elements. If the sloped-line segment is tangent to the real diode curve at the Q-point, this approximate circuit has the same small-signal circuit at the Q-point as the real diode.

3.3.4 Diode in Small Signal Circuits

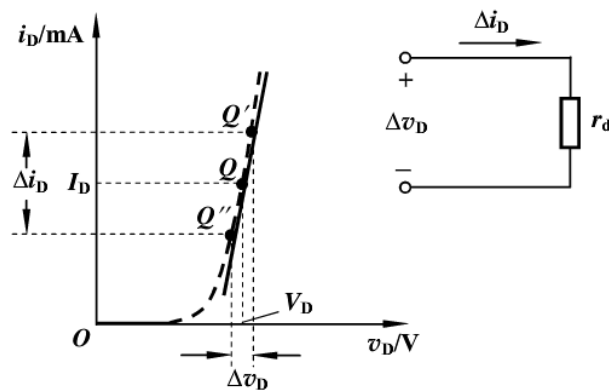


Figure 3.5: I-V Characteristic of Diode in Small Signal

$$r_d = \frac{1}{g_d} = \frac{V_T}{I_{DQ}}$$

Where, in the condition of $T = 300$ K,

$$V_T = 26 \text{ mV}$$

3.4 Applications of Diodes

3.4.1 Rectifier Circuit

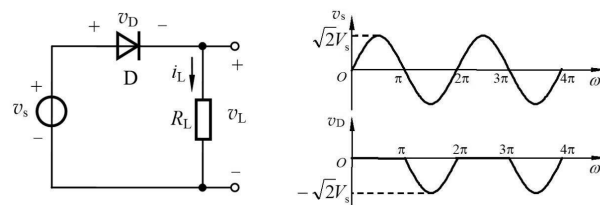


Figure 3.6: A Simple Rectifier Circuit

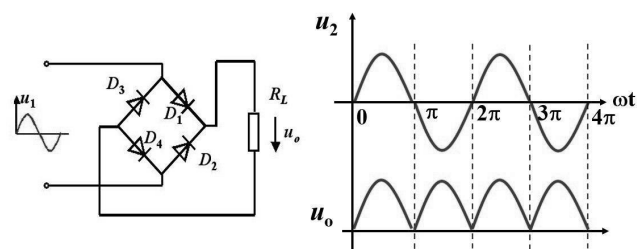


Figure 3.7: A Bridged Rectifier Circuit

3.4.2 Limiting Circuit

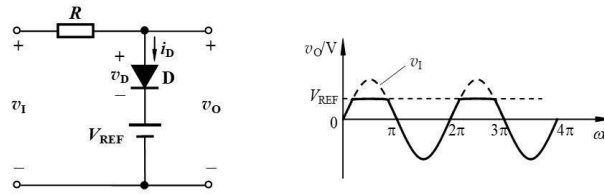
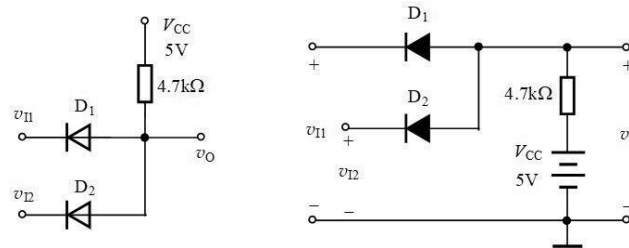


Figure 3.8: A Limiting Circuit

3.4.3 Switching Circuit

Figure 3.9: A Switching Circuit, $v_o = 5 \text{ V}$ holds only if all the input voltage is 5 V

3.5 Diodes for Special Usage

3.5.1 Zener diode

A Zener diode is manufactured to be broken-through. It is used to stabilize voltages. As we can know from the I-V characteristic of an diode, when the diode is broken-through, change in current only cause little change in voltage.

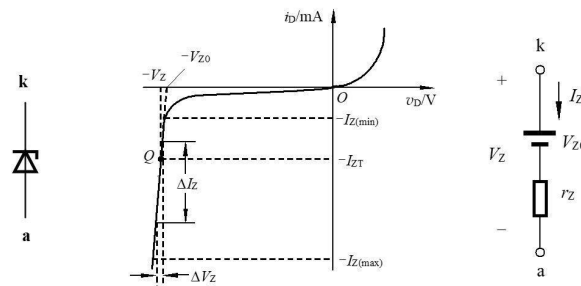


Figure 3.10: Zener Diode's electronic symbol and I-V characteristic

3.5.2 Photodiode

A photodiode is a semiconductor device that converts light into an electrical current. The current is generated when photons are absorbed in the photodiode.

3.5.3 Light-emitting diode

A light-emitting diode (LED) is a semiconductor light source that emits light when current flows through it.

3.5.4 Schottky diode

The Schottky diode (named after the German physicist Walter H. Schottky), also known as Schottky barrier diode or hot-carrier diode, is a semiconductor diode formed by the junction of a semiconductor with a metal. It has a low forward voltage drop and a very fast switching action.

Chapter 4

MOSFET and Amplifying Circuit

4.1 Classification of MOSFET


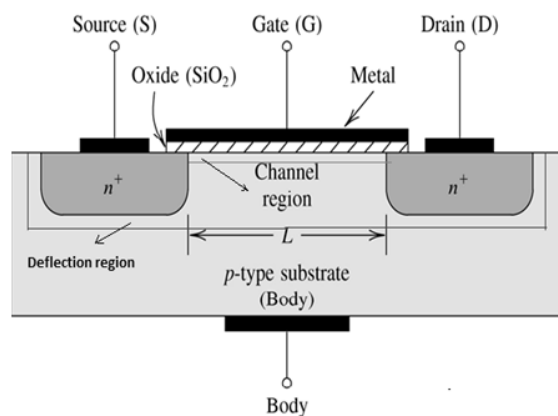


Figure 4.1: MOSFET Block diagram

4.1.1 N-type Enhancement-mode MOSFET

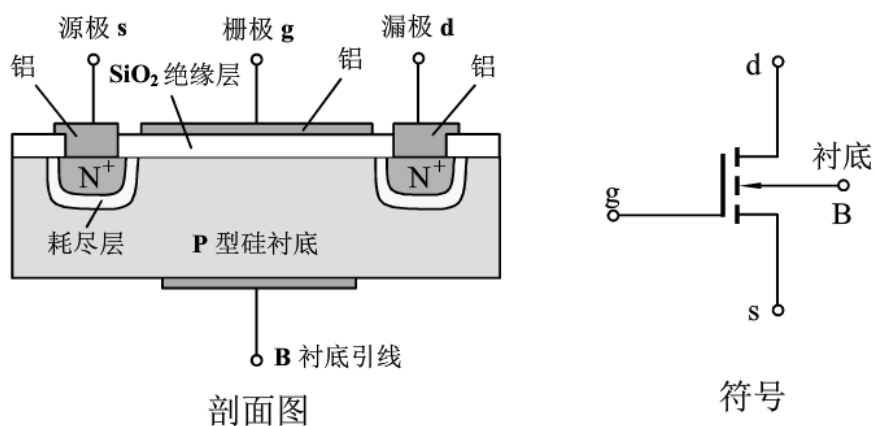

Only when $V_{GS} > V_{TN} > 0$, N-Channel will be formed, MOSFET is conductive. V_{TN} is called the Threshold Voltage.


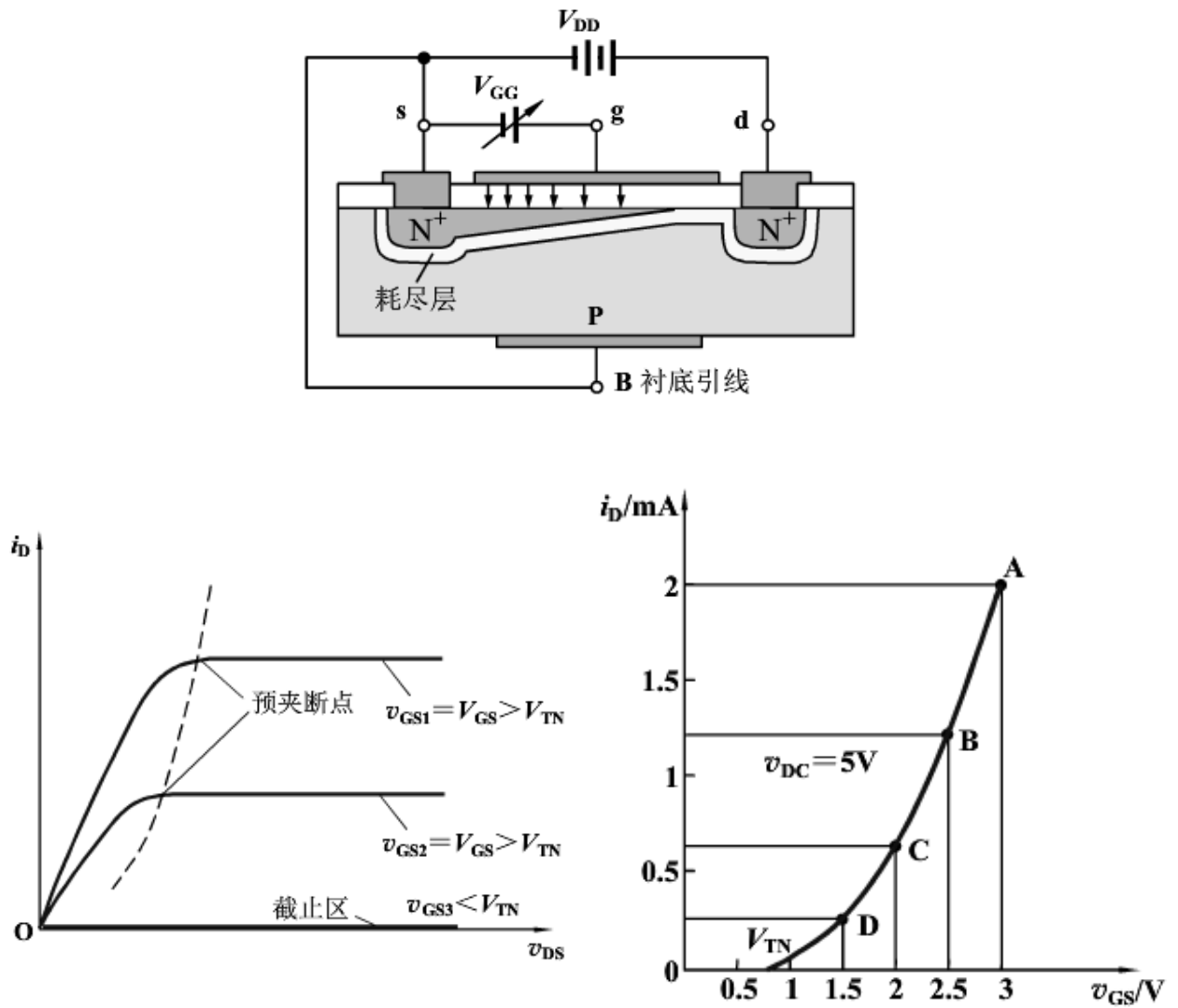


Figure 4.2: The I-V Characteristic of N-type Enhancement-mode MOSFET

4.1.2 N-type Depletion-mode MOSFET

The only difference between Enhancement-mode and Depletion-mode is the charges in oxide, which made $V_{TN} < 0$

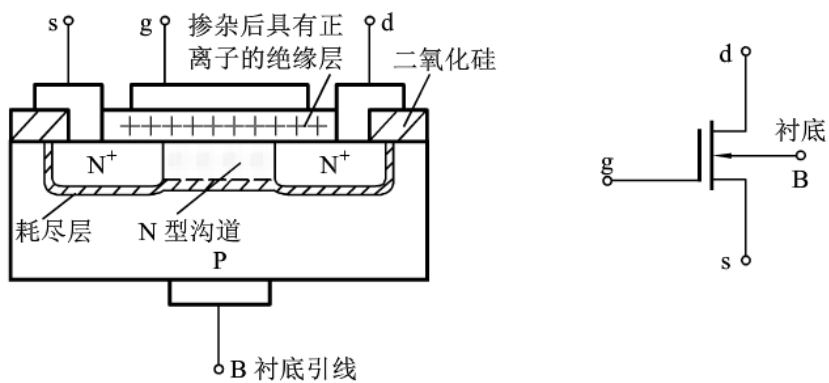


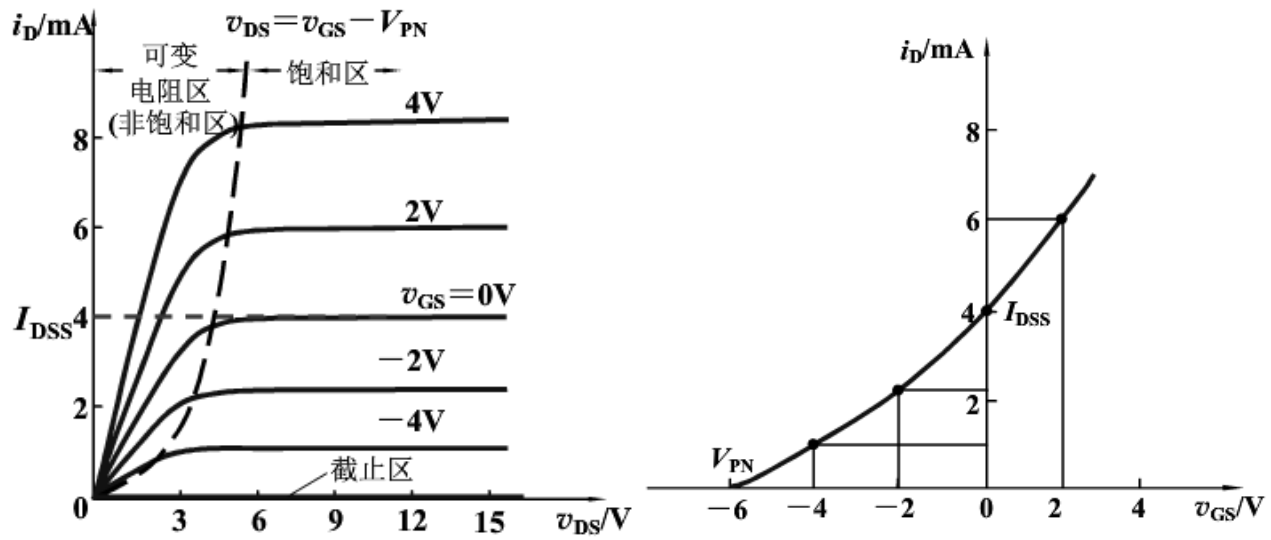


Figure 4.3: The I-V Characteristic of N-type Depletion-mode MOSFET

4.1.3 P-type MOSFET

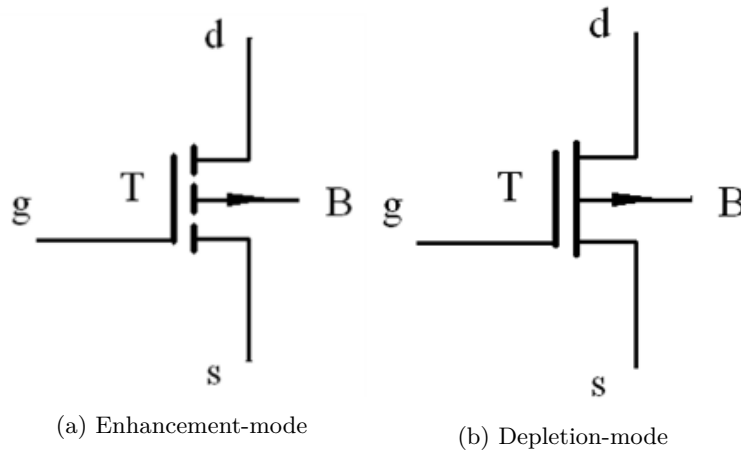

(a) Enhancement-mode

(b) Depletion-mode

Figure 4.4: The Electronic Symbol of P-type MOSFET


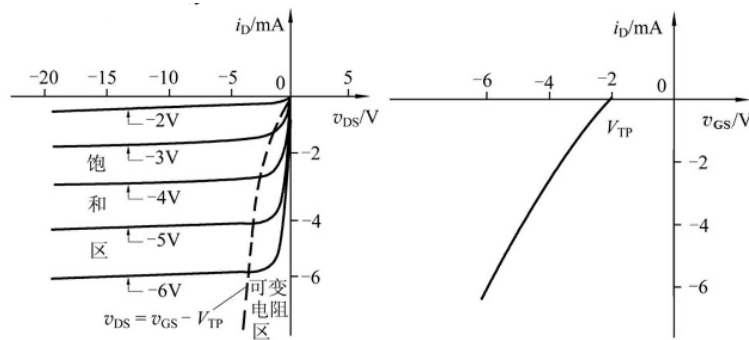


Figure 4.5: The I-V Characteristic of N-type Depletion-mode MOSFET

4.2 Static Working Point

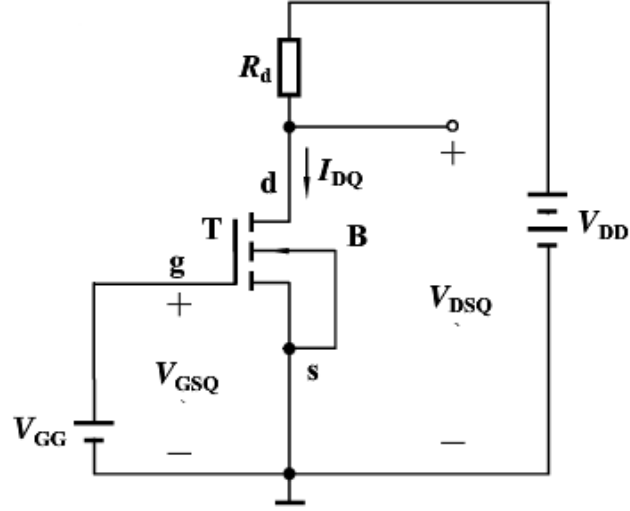

To calculate the static working point of a MOSFET

$$\begin{cases} V_{GSQ} = V_{GG} \\ I_{DQ} = K_n (V_{GSQ} - V_{TN})^2 \\ V_{DSQ} = V_{DD} - I_{DQ} R_d \end{cases}$$

Note that $V_{DSQ} > V_{GSQ} - V_{TN}$ must be verified to ensure that MOSFET is working in active mode. Then for small AC signal, the current at drain is

$$i_D = 2K_n (V_{GSQ} - V_{TN}) v_{GS} = g_m v_{GS}$$

4.3 Early Effect

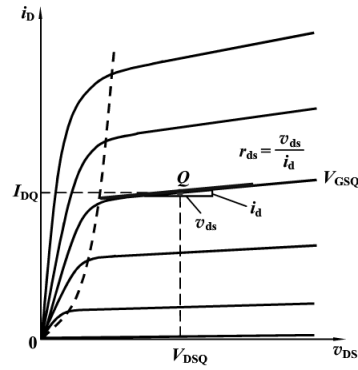


Figure 4.6: MOSFET-Early-Effect

$$i_D = K_n (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS})$$


$$r_{ds} = \left. \frac{\partial v_{DS}}{\partial i_D} \right|_{V_{GSQ}} = \frac{1}{\lambda K_n (V_{GSQ} - V_{TN})^2} \approx \frac{1}{\lambda I_{DQ}} = \frac{V_A}{I_{DQ}}$$

Where V_A is called the Early Voltage

$$V_A = \frac{1}{\lambda}$$


4.4 Three types of Amplifier Circuit

4.4.1 Common Source Amplifier Circuit

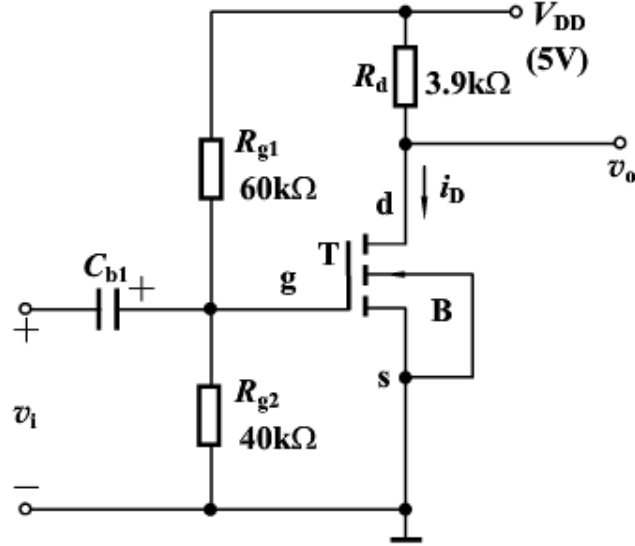

$$\begin{cases} V_{GSQ} = \left(\frac{R_{g2}}{R_{g1} + R_{g2}} \right) V_{DD} \\ I_{DQ} = K_n (V_{GSQ} - V_{TN})^2 \\ V_{DSQ} = V_{DD} - I_{DQ} R_d \end{cases}$$

$$g_m = 2K_n (V_{GSQ} - V_{TN})$$

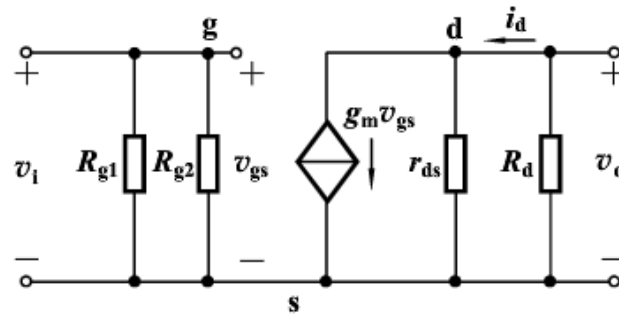


$$A_v = -g_m (r_{ds} \parallel R_d)$$

$$R_i = R_{gs1} \parallel R_{gs2}$$


$$R_o = R_d \parallel R_d \approx R_d$$

4.4.2 Common Drain Amplifier Circuit

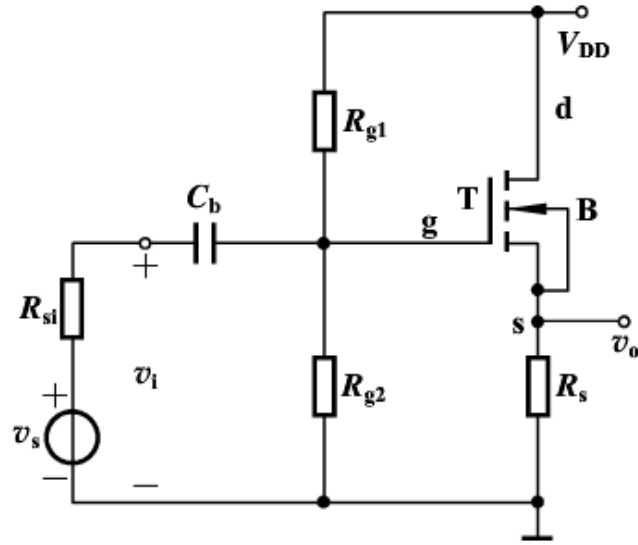

$$\begin{cases} V_{GSQ} = \frac{R_{g2}}{R_{g1} + R_{g2}} \cdot V_{DD} - I_{DQ} R_s \\ I_{DQ} = K_n (V_{GSQ} - V_{TN})^2 \\ V_{DSQ} = V_{DD} - I_{DQ} R_s \end{cases}$$

$$g_m = 2K_n (V_{GSQ} - V_{TN})$$

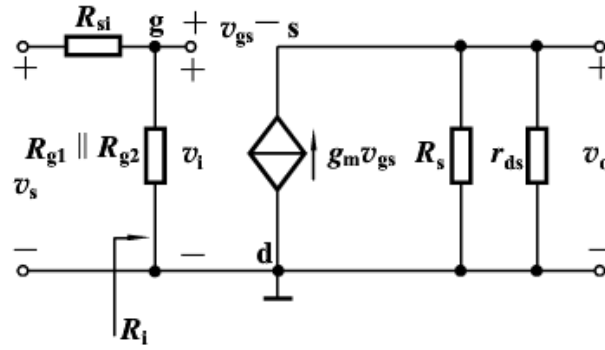


$$A_v = \frac{g_m (R_s \parallel r_{ds})}{1 + g_m (R_s \parallel r_{ds})} \approx 1$$

$$R_i = R_{g1} \parallel R_{g2}$$


$$R_o = R_s \parallel r_{ds} \parallel \frac{1}{g_m}$$

4.4.3 Common Gate Amplifier Circuit

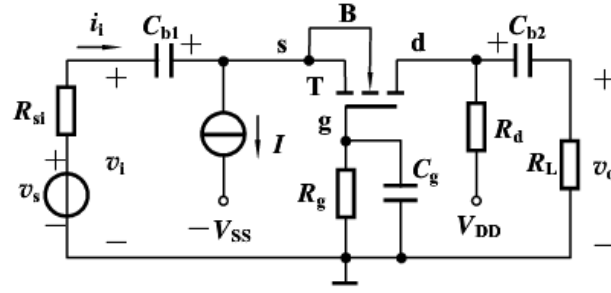

$$\begin{cases} I_{DQ} = K_n (V_{GSQ} - V_{TN})^2 = I \\ V_{DSQ} = V_{DD} - I_{DQ} R_d + V_{GSQ} \end{cases}$$

$$g_m = 2K_n (V_{GSQ} - V_{TN})$$

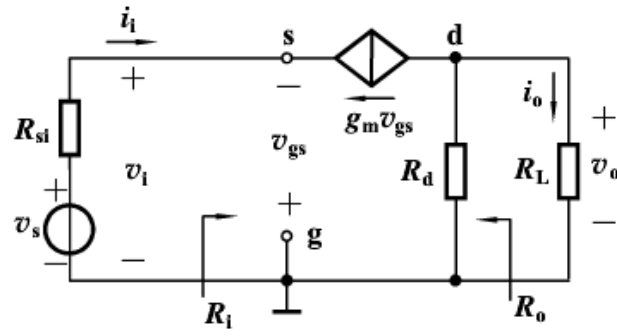

$$A_v = g_m (R_d \parallel R_L)$$


$$R_i \approx \frac{1}{g_m}$$

$$R_o \approx R_d$$

Chapter 5

Bipolar Junction Transistor


5.1 Control Principle

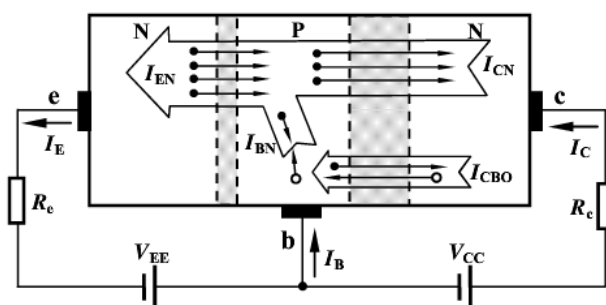

$$\alpha = \frac{I_{CN}}{I_E}$$


$$\beta = \frac{I_{CN}}{I_{CBO}}$$

5.2 Three Types of Amplifier Circuit

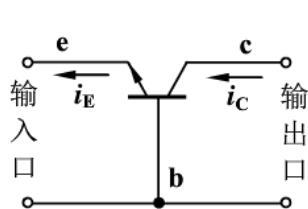


(a) 共基极

$$i_C = \alpha i_E$$

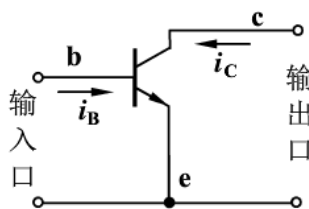

(b) 共发射极


$$i_C = \beta i_B$$

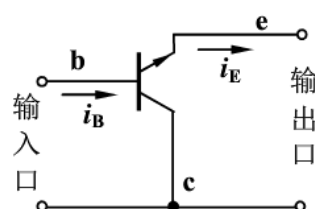

(c) 共集电极

$$i_E = (1 + \beta) i_B$$

5.3 Static Working Point

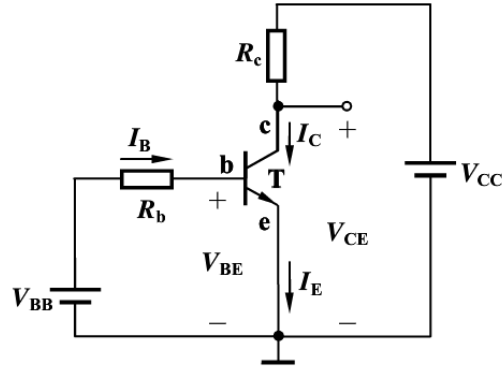

$$I_{BQ} = \frac{V_{BB} - V_{BEQ}}{R_b}$$


$$V_{BEQ} = 0.7 \text{ V}$$

$$I_{CQ} = \beta I_{BQ}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_c$$

Note that the static working point is not associated with small signals discussed below.

5.4 Model of Small Signal

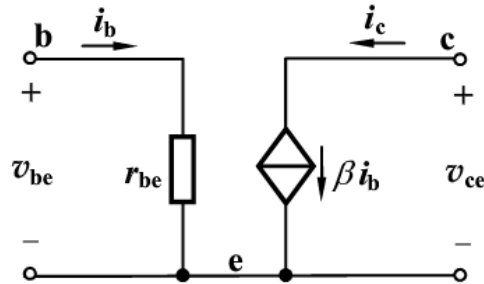

When $T = 300 \text{ K}$

$$r_{be} = 200 \, \Omega + (1 + \beta) \frac{26 \text{ mV}}{I_{CQ} (\text{mA})}$$

5.5 Compound Transistor

