


Homework for Chapter 2

Xiping Hu

<http://thehxp.tech/>

March 15, 2020

2.4.4 INA2128 型仪用放大器电路如图题 2.4.4 所示, 其中 R_1 是外接电阻。(1) 它的输入干扰电压 $V_c =$

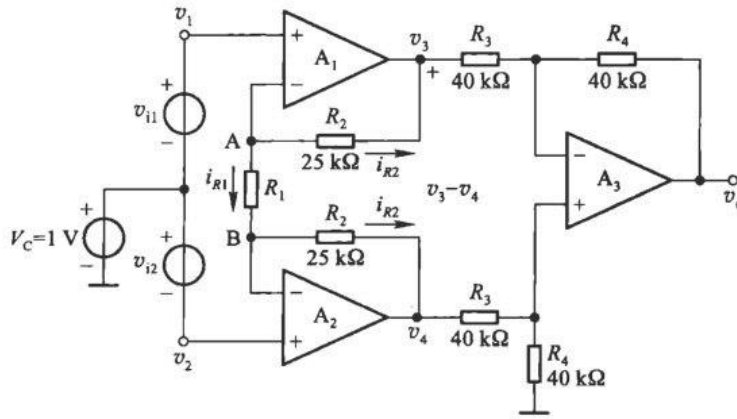

图题 2.4.4

1 V (直流), 输入信号 $v_{i1} = -v_{i2} = 0.04 \sin \omega t$ V, 输入端电压 $v_1 = (V_c + 0.04 \sin \omega t)$ V, $v_2 = (V_c - 0.04 \sin \omega t)$ V, 当 $R_1 = 1$ kΩ 时, 求出 v_3 、 v_4 、 $v_3 - v_4$ 和 v_o 的电压值; (2) 当输入电压 $V_{id} = V_1 - V_2 = 0.01866$ V 时, 要求 $V_o = -5$ V, 求此时外接电阻 R_1 的阻值。

Solution for Q1 Since A_1 and A_2 are ideal operational amplifiers

$$v_A = v_1 = V_c + v_{i1}$$

$$v_B = v_2 = V_c - v_{i2}$$

Now we currents around A_2 can be calculated

$$i_{R2} = i_{R1} = \frac{v_A - v_B}{R_1} = \frac{v_{i1} + v_{i2}}{R_1} = 0.08 \sin \omega t \text{ mA}$$

$$v_3 = v_A + i_{R2} R_2 = (1 + 2.04 \sin \omega t) \text{ V}$$

$$v_4 = v_B - i_{R2} R_2 = (1 - 2.04 \sin \omega t) \text{ V}$$

(I noted that the arrow below the first R_2 counted from top to bottom might be opposed)

We can then calculate the input voltage of A_3

$$V_{A3_{input}} = \frac{R_4}{R_3 + R_4} v_4 = (0.5 - 1.02 \sin \omega t) \text{ V}$$

For R_4 , I assume the current direction is from left to right.

$$i_{R4} = \frac{v_3 - V_{A3_{input}}}{R_3} = \frac{0.5 + 3.06 \sin \omega t \text{ V}}{40 \text{ k}\Omega}$$

Finally

$$v_o = V_{A3_{input}} - i_{R4} R_4 = -4.08 \sin \omega t \text{ V}$$

Solution for Q2 Since A_1 and A_2 are ideal operational amplifiers

$$v_A = v_1 = V_C + v_{i1}$$

$$v_B = v_2 = V_C - v_{i2}$$

Now we currents around A_2 can be calculated

$$i_{R2} = i_{R1} = \frac{v_A - v_B}{R_1} = \frac{v_{i1} + v_{i2}}{R_1}$$

$$v_3 = v_A + i_{R2} R_2 = V_C + v_{i1} + \frac{v_{i1} + v_{i2}}{R_1} R_2$$

$$v_4 = v_B - i_{R2} R_2 = V_C - v_{i2} - \frac{v_{i1} + v_{i2}}{R_1} R_2$$

(I noted that the arrow below the first R_2 counted from top to bottom might be opposed)

We can then calculate the input voltage of A_3

$$V_{A3_{input}} = \frac{R_4}{R_3 + R_4} v_4 = \frac{R_4}{R_3 + R_4} \left(V_C - v_{i2} - \frac{v_{i1} + v_{i2}}{R_1} R_2 \right)$$

For R_4 , I assume the current direction is from left to right.

$$i_{R4} = \frac{v_3 - V_{A3_{input}}}{R_3} = \frac{\left(V_C - v_{i2} - \frac{v_{i1} + v_{i2}}{R_1} R_2 \right) - \frac{R_4}{R_3 + R_4} \left(V_C - v_{i2} - \frac{v_{i1} + v_{i2}}{R_1} R_2 \right)}{R_3}$$

Finally

$$\begin{aligned} v_o &= V_{A3_{input}} - i_{R4} R_4 \\ &= \frac{R_4}{R_3 + R_4} \left(V_C - v_{i2} - \frac{v_{i1} + v_{i2}}{R_1} R_2 \right) \\ &\quad - \frac{\left(V_C - v_{i2} - \frac{v_{i1} + v_{i2}}{R_1} R_2 \right) - \frac{R_4}{R_3 + R_4} \left(V_C - v_{i2} - \frac{v_{i1} + v_{i2}}{R_1} R_2 \right)}{R_3} R_4 \end{aligned}$$

When $V_1 - V_2 = v_{i1} + v_{i2} = 0.01866 \text{ V}$, $v_o = 5 \text{ V}$, we can solve for R_1

$$R_1 = 186 \text{ }\Omega$$