

Homework for Analogue Electronics

Xiping Hu

<http://thehxp.tech/>

February 25, 2020

5、
求图 5 电路中 b 点的电位。


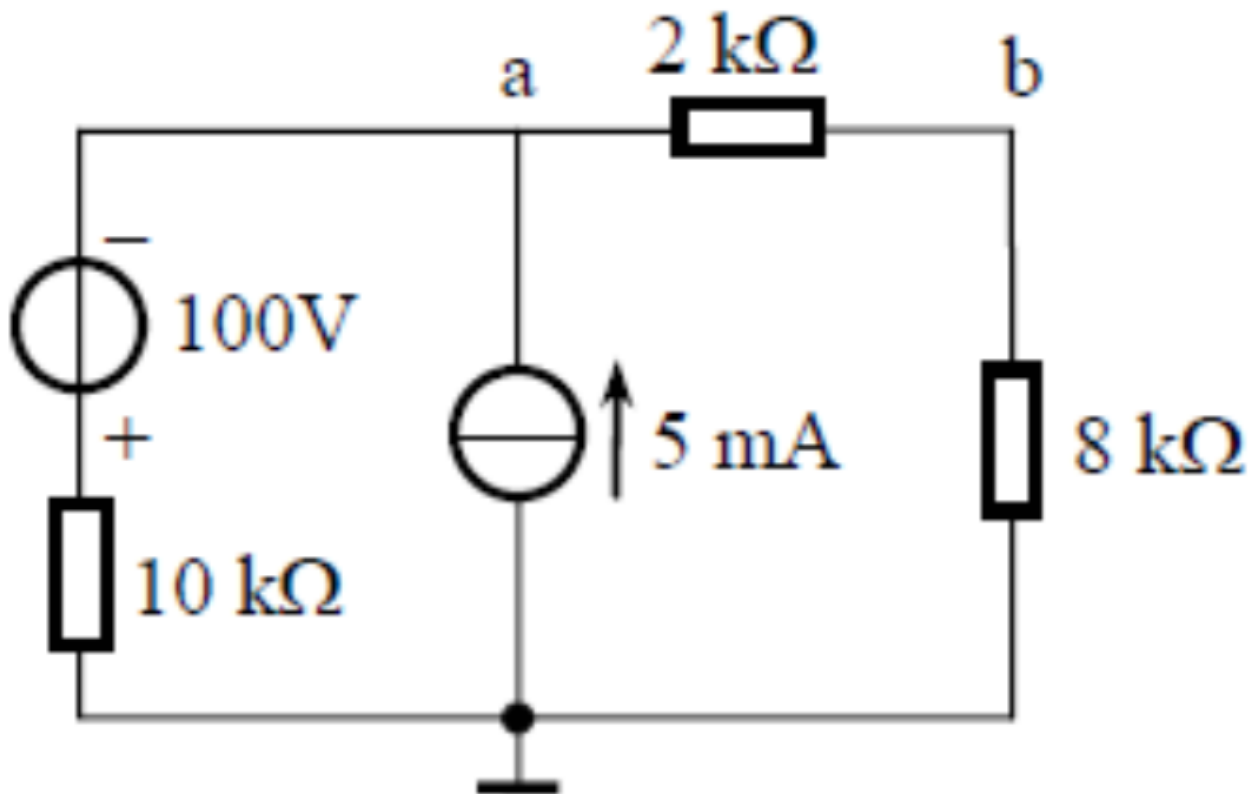


图 5

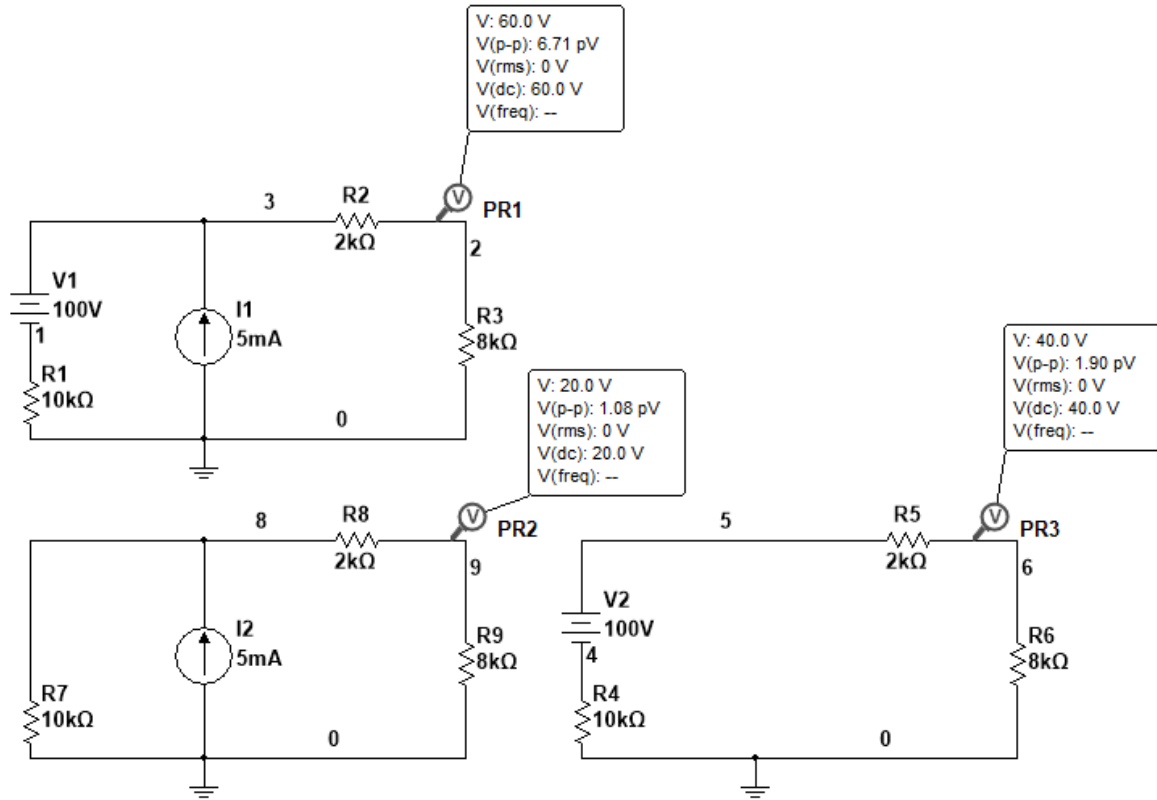Solution We separate the whole circuit into these two sub-circuits, as the picture below shows.



For the circuit on the bottom left position, we write

$$I = 5 \text{ mA} \times \frac{10 \text{ k}\Omega}{2 \text{ k}\Omega + 8 \text{ k}\Omega + 10 \text{ k}\Omega} = 2.5 \text{ mA}$$

$$U = IR = 2.5 \text{ mA} \times 8 \text{ k}\Omega = 20 \text{ V}$$

For the circuit on the bottom right

$$I = \frac{100 \text{ V}}{10 \text{ k}\Omega + 2 \text{ k}\Omega + 8 \text{ k}\Omega} = 5 \text{ mA}$$

$$U = 5 \text{ mA} \times 8 \text{ k}\Omega = 40 \text{ V}$$

So, as for the original circuit

$$U_b = 20 \text{ V} + 40 \text{ V} = 60 \text{ V}$$